



12169

13141

3 Hours/100 Marks

Seat No.

--	--	--	--	--	--	--	--	--	--

- Instructions:**
- (1) **All** questions are **compulsory**.
 - (2) Answer **each** next main question on a **new** page.
 - (3) Figures to the **right** indicate **full** marks.
 - (4) Use of Non-programmable Electronic Pocket Calculator is **permissible**.
 - (5) Mobile Phone, Pager and any other Electronic Communication devices are **not** permissible in Examination Hall.

MARKS
12

1. A) Attempt **any three** of the following :

1) State Ohm's law. Calculate current 'I', delivered by battery in Fig. 1.

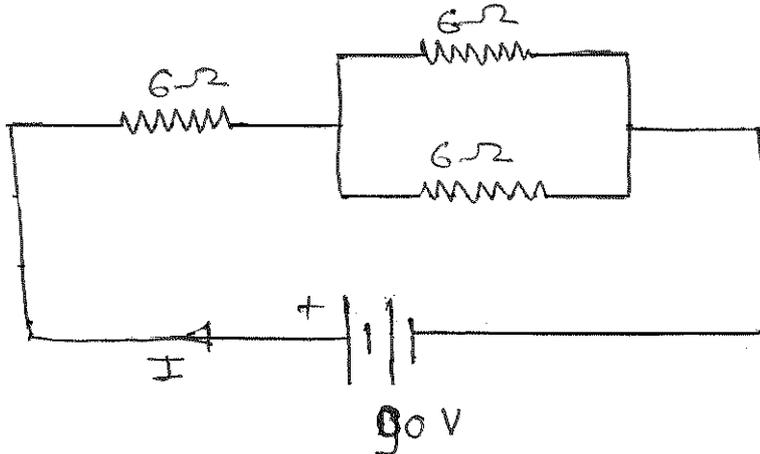


Fig. 1

- 2) Explain with the diagram wiring Harness.
- 3) What is Intrinsic and Extrinsic semiconductor ?
- 4) Differentiate between core type and shell type transformer.

B) Attempt **any one** of the following :

6

- 1) Explain speed control methods of D.C. shunt and series motor.
- 2) State working principle of transformer, A 1ϕ , 50 Hz transformer has 300 primary and 750 secondary turns. The net cross-sectional area of the core is 64 cm^2 . If the primary induced e.m.f. is 440 V, Find.
 - i) Maximum Flux density in the core.
 - ii) E.M.F. induced in the secondary.

2. Attempt **any four** of the following :

16

- 1) Draw power triangle. Define active and reactive power. State units of both the power.
- 2) Explain working of LVDT with diagram.

P.T.O.



- 3) Explain working of PN junction with ac voltage.
 - 4) Draw and explain wiring diagram of turn indicator.
 - 5) Define
 - i) Waveform
 - ii) Frequency
 - iii) Time period
 - iv) Amplitude
 - 6) Explain operation of load cell with diagram.
3. Attempt **any four** of the following : 16
- 1) Define transducer. Classify the transducers.
 - 2) Explain the working of ultrasonic flowmeter with diagram.
 - 3) Draw symbols of NAND, NOR, AND, NOT logic gates. Give their Truth Tables and logic equations.
 - 4) State Faraday's laws of electromagnetic induction. Define Flux density and magnetic Flux.
 - 5) Explain with truth table, RS Flip Flop.
4. A) Attempt **any three** of the following : 12
- 1) What are the precautions to be taken while using measuring instruments ?
 - 2) Draw the circuit diagram of bridge rectifier. Explain its operation.
 - 3) Draw and explain Hot Wire anemometer.
 - 4) Draw any four symbols of electrical circuit used for automobile.
- B) Attempt **any one** of the following : 6
- 1) Draw and explain general measurement system.
 - 2) Draw a neat sketch of multipolar D.C. Motor. Write function of any four parts.
5. Attempt **any four** of the following : 16
- 1) Compare insulated and ground return system. Which is advisable ? Why ?
 - 2) Explain transistor as an amplifier.
 - 3) Draw neat diagram and explain common anode 7 segment LED display.
 - 4) Give symbol and explain working of photodiode.
 - 5) Enlist different temperature transducer. Explain measurement of temperature using thermistor.
 - 6) Draw and explain characteristics of D.C. shunt motor.
6. Attempt **any four** of the following : 16
- 1) Why filter is necessary in rectification ? What are different types of filters.
 - 2) Explain operation of 4 : 1 MUX with truth table.
 - 3) What is shift register ? Explain working with diagram.
 - 4) State different types of stepper motor. Give four applications of it.
 - 5) Differentiate between electrical and mechanical instruments.
-