



12169

21314

3 Hours/100 Marks

Seat No.

--	--	--	--	--	--	--	--	--	--

- Instructions :** (1) **All** questions are **compulsory**.
(2) **Illustrate** your answers with neat sketches **wherever** necessary.
(3) Figures to the **right** indicate **full** marks.
(4) **Assume** suitable data, **if** necessary.
(5) **Use** of Non-programmable Electronic Pocket Calculator is **permissible**.
(6) Mobile phone, pager and **any** other electronic communication devices are **not permissible** in Examination Hall.

MARKS

1. Attempt **any ten** of the following :

20

- State Ohm's law and write equation for finding current.
- Write the principle on which transformer works.
- State two applications of stepper motor.
- What is positive and negative return system.
- Define analog signal and digital signal.
- Draw the symbol of NOR and NAND gate.
- What is LVDT ? State two application of it.
- Draw symbol and construction of NPN transistor.
- State the working principle of AC motor.
- List the two application of zener diode, also draw symbol of it.
- Write names of different photoelectric type transducer.
- Write working of seven segment LED display.

P.T.O.



2. Attempt **any four** of the following : **16**
- a) Explain the importance of colour coding in a automobile wiring.
 - b) Draw and explain the phasor diagrams for purely resistive and purely inductive circuit.
 - c) State the different transducers used for temperature measurement and explain working principle of any one type.
 - d) With neat circuit diagram, draw forward and reverse characteristic of P-N junction diode.
 - e) Explain operating principle of alternator.
 - f) Explain working of 4 : 1 multiplexer with logic diagram.
3. Attempt **any four** of the following : **16**
- a) Draw logic circuit of 2 : 4 decoder and explain with truth table.
 - b) A single-phase transformer has 350 primary and 1050 secondary turns. The primary is connected to a 400 V, 50 Hz supply. If the net cross-sectional area of core is 50 cm², find
 - i) the maximum value of flux density in the core
 - ii) voltage induced in the secondary winding.
 - c) Why symbols are necessary in Electrical Engineering ? State necessity of wiring harness.
 - d) Draw symbols of OR, AND logic gates with their truth table.
 - e) With neat diagram explain working of ultrasonic flow meter.
 - f) Draw neat diagram of bridge rectifier. Explain its working with input-output waveforms.
4. Attempt **any four** of the following : **16**
- a) Compare core type and shell type transformer on the basis of
 - i) Capacity
 - ii) Construction
 - iii) Cost
 - iv) Application.



MARKS

- b) Draw speed-torque characteristics of (i) D.C. series motor (ii) D.C. shunt motor.
- c) Write four applications of shift registers and counters.
- d) Explain measurement of force by load cell with diagram.
- e) Compare insulated and ground return system (any four parameters).
- f) Draw symbols of LED, SCR, TRIAC, PNP transistor.

5. Attempt **any four** of the following :

16

- a) Define the following terms :
 - i) Permeability
 - ii) Reluctance
 - iii) Magnetic field intensity
 - iv) Magnetic flux.
- b) Explain battery ignition and magneto ignition.
- c) What are the main parts of D.C. motors ? State the function of each part.
- d) State the working principle of piezo-electric transducer with diagram.
- e) Explain the working principle of contact less electrical tachometer.
- f) Draw symbol and working of phototransistor. Also state two application of it.

6. Attempt **any four** of the following :

16

- a) Draw connection diagram of ammeter, voltmeter for a DC load. Write any four applications of multimeter.
- b) What is oscillator ? Write its four applications.
- c) Explain concept of electrical method for moisture measurement.



- d) Define the following terms :
- i) Power factor
 - ii) Reactive power
 - iii) Frequency
 - iv) Resistance.
- e) Draw neat circuit diagram of common emitter amplifier. Draw neat V-I characteristics of SCR and state its two application.
- f) Write four difference between mechanical and electrical/electronic instruments.
-